

# END TERM EXAMINATION

FOURTH SEMESTER [B.TECH] JUNE 2025

Paper Code: EEC-208

Subject: Circuits and Systems

Time: 3 Hours



Maximum Marks: 60

Note: Attempt five questions in all including Q.No.1 which is compulsory. Select one question from each unit. Assume missing data, if any.

Q1 Attempt any four of the following questions:

(4×5=20)

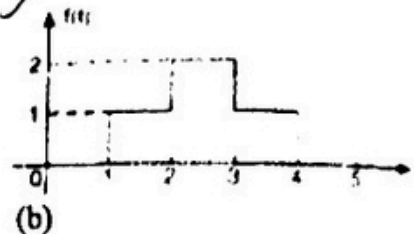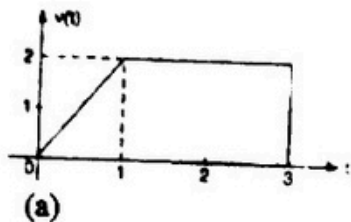
- a) Define and classify signals with suitable examples.
- b) State and explain Laplace Transform properties.
- c) Derive the differential equation of an RLC series circuit.
- d) Obtain the Laplace transform of  $e^{-at} \sin \omega t$  and  $1 - e^{-at}$  where  $a$  is constant.
- e) Synthesize the waveforms:



- f) Define and explain two-port parameters.
- g) What are the key differences between z-Transform and Laplace Transform?
- h) Explain any two properties of network functions.

## UNIT-I

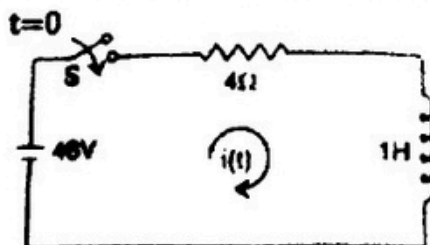- Q2 a) Define LTI systems and discuss their characteristics. (5)
- b) Consider the R-L circuit with  $R=4\Omega$  and  $L=1H$  excited by a 48V d.c. source as shown in figure. Assume the initial current through the inductor is 3A. Using the Laplace transform determine the current  $i(t)$ ;  $t \geq 0$ . Also draw the s-domain representation of the circuit. (5)



OR

- Q3 a) Explain the concept of state space analysis with an example. (5)
- b) Discuss the properties of z-Transform. (5)


## UNIT-II

- Q4 a) Find the transient response of an RLC circuit for a step input using Laplace Transform. (5)
- b) Determine  $f(0^+)$  and  $f(\infty)$  for the following function: (5)

$$F(s) = \frac{5s^3 - 1600}{s(s^3 + 18s^2 + 90s + 800)}$$

**OR**

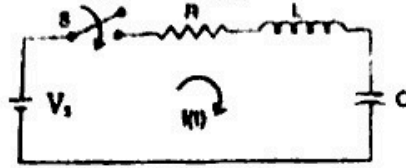
- Q5 a) Consider the RLC series circuit shown in figure.  $V_s = 2V$ ;  $R = 6\Omega$ ;  $L = 2H$ ;  $C = 0.25F$ . Determine  $i(0^+)$ ;  $\frac{di}{dt}(0^+)$ ;  $\frac{d^2i}{dt^2}(0^+)$  and  $i(t)$ . (5)



- b) Without finding the inverse Laplace transform of  $F(s)$ , determine  $f(0^+)$  and  $f(\infty)$  for each of the following functions: (5)
- (i)  $F(s) = \frac{4e^{-2s}(s+50)}{s}$  (ii)  $F(s) = \frac{s^2+6}{s^2+7}$

**UNIT-III**

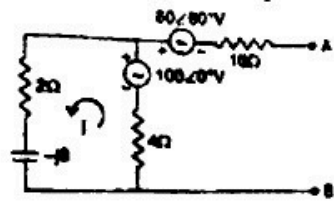
- Q6 a) Find the Thevenin's equivalent circuit at terminals AB of the given circuit. (5)



- b) Explain the Y-Δ (Star-Delta) and Δ-Y (Delta-Star) transformations. Provide the formulas used for the conversion. (5)

**OR**

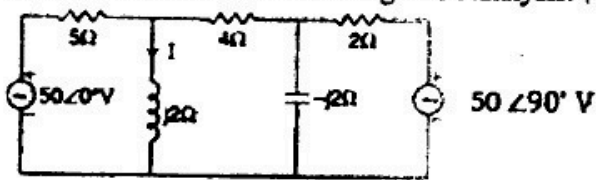- Q7 a) State and explain Thevenin's and Norton's theorems. How are these theorems applied to simplify complex AC circuits? (5)
- b) Find current I in the circuit using mesh analysis. <https://www.ggsipuonline.com> (5)



**UNIT-IV**

- Q8 a) Define ABCD parameters and explain their significance. (5)
- b) Derive the condition for reciprocity and symmetry in case of (a) T parameters and (b) h parameters (5)

**OR**

- Q9 a) Obtain the Z parameters of the network in terms of ABCD and hybrid parameters. (5)
- b) Explain how Hurwitz polynomial is used in network analysis. (5)

\*\*\*\*\*